


ECE 449 Project



University
of Victoria

Pinout of Processor


- Interrupt is **optional**

 

Resets

- Reset and execute causes the system to execute the user's code
- Reset and load causes the system to load the user's code into RAM
- Explanations and detailed specifications will follow in slide 7

System Description

 

Comments on the system architecture -RAM

- A dual ported RAM is used to ensure that instruction and data traffic is separated (Harvard architecture)
- The RAM serializes the access requests arbitrarily.
- The suggested (slide 9) RAM implementation is a synchronous one and it allows the specification of the delay (in clock cycles) of the read data to appear on the data_out port.

Comments on the system architecture -ROM

- ROM is used to store a rudimental BIOS.
- ROM and its BIOS will be provided to you
- The main functionality of the BIOS is
 - Load user code into the appropriate location in RAM
 - Execute user code

Resets

- The two resets implement the load and execute functionality of the BIOS
- Both clear the PC
- **Reset and Execute** *vectors* to address 0x0000 while **Reset and Load** *vectors* to address 0x0002.
- At each address, the developer has introduced the appropriate branch (BRR) instruction that vectors to the reset-handling routine (this is part of the BIOS)

ROM, RAM and ports

- ROM is 1024-byte large starting at address 0x0000
- RAM is a 1024 byte block starting at address 0x0400
- We use memory-mapped ports. The input port is located at 0xFFFF0 while the output port is at 0xFFFF1

RAM module

- Please use the dual port distributed RAM macro `XPM_MEMORY_DPDISTRAM` from Xilinx XPM macro group
- This macro can configure a dual ported memory where port A can be used for both reading and writing while port B can only be used for reading only (from memory).

Instruction Format


- Three types of instructions
 - A-Format
 - e.g. arithmetic instructions
 - B-Format
 - e.g. branch instructions
 - L-Format
 - e.g. load and store instructions

A-Format Instructions


Arithmetic Instructions:




Format A0

 

Format A1

 


Format A2

 

Format A3


e.g.:

ADD r3,r2,r1

 


B-Format Instructions

Branch Instructions:

 


Format B1

 

Format B2

e.g.:

BR r3+0x8

 

Subroutine

...

...

BR.SUB r2+072

...

subroutine:

...

return

Subroutine

- Register r7 plays the additional role of a Link Register used in subroutine call&return

- **BR.SUB rx+disp**

The current program counter is placed in r7 while the PC is loaded with the target address (i.e. $(rx)+2*disp$)

...

...


0X1A: **BR.SUB**

0X1C: ...

subroutine:

...

return

 

For the PC operations, the argument is the value of the PC just before the instruction is fetched, while the result is the value of the PC at the conclusion of the execution of the instruction.

Subroutine

- LR: a dedicated register for br.sub instructions
 - br.sub: PC+2 is loaded into r7
 - return: PC is loaded with r7

```
...  
...  
0X1A: BR.SUB  
0X1C: ...  
  
subroutine:  
...  
0X88: return
```


```
PC: 8A  
  
r7: 1C
```

The contents of PC shown are those immediately after return was fetched

Subroutine

- LR: a dedicated register for br.sub instructions
 - br.sub: PC+2 is loaded into r7
 - return: PC is loaded with r7

 
```
...  
...  
0X1A: BR.SUB  
0X1C: ...  
  
subroutine:  
...  
0X88: return
```




The contents of PC shown are those immediately after return completed execution

L-Format

● Load/Store Instructions

 

Format L.1

 


Format L.2

e.g.: **LOAD r1,@r2**

or **LOAD r.dest,r.src**

LOAD r1,r2

 


Project

- **A processor that executes every program written in the instruction set**


Processor Architecture

 - 1)Datapath
 - Includes components, alu, register file, memory, ...
- 2)Controller
 - Controls flow of instruction and data in datapath



Instruction Memory

We need a container to hold instructions

 

Please see slide 4 and subsequent discussing memory specifications

Register File

A place for r0...r7

Memory

Reg File

Alu

A unit for arithmetic calculations

Memory

Reg File

ALU

Data Memory

A unit that holds data

Memory

Reg File


ALU

Memory

Pipeline Architecture

To break critical path

Instruction
Fetch

 


Decode



Execute




Memory
Access

 

Write
Back

5-Stages Datapath


Up to now, design of main components

 

5-Stages Datapath

Up to now, design of main components

 Complete the datapath for every instruction gradually




5-Stages Datapath

Up to now, design of main components


Complete the datapath for every instruction gradually

e.g. ADD instruction

 


PC

 
A component that holds address of Inst. Memory (PC)



Fetch

 

ADD

 


Decode


IF/ID Register

ID/EX


Decode

 


ADD

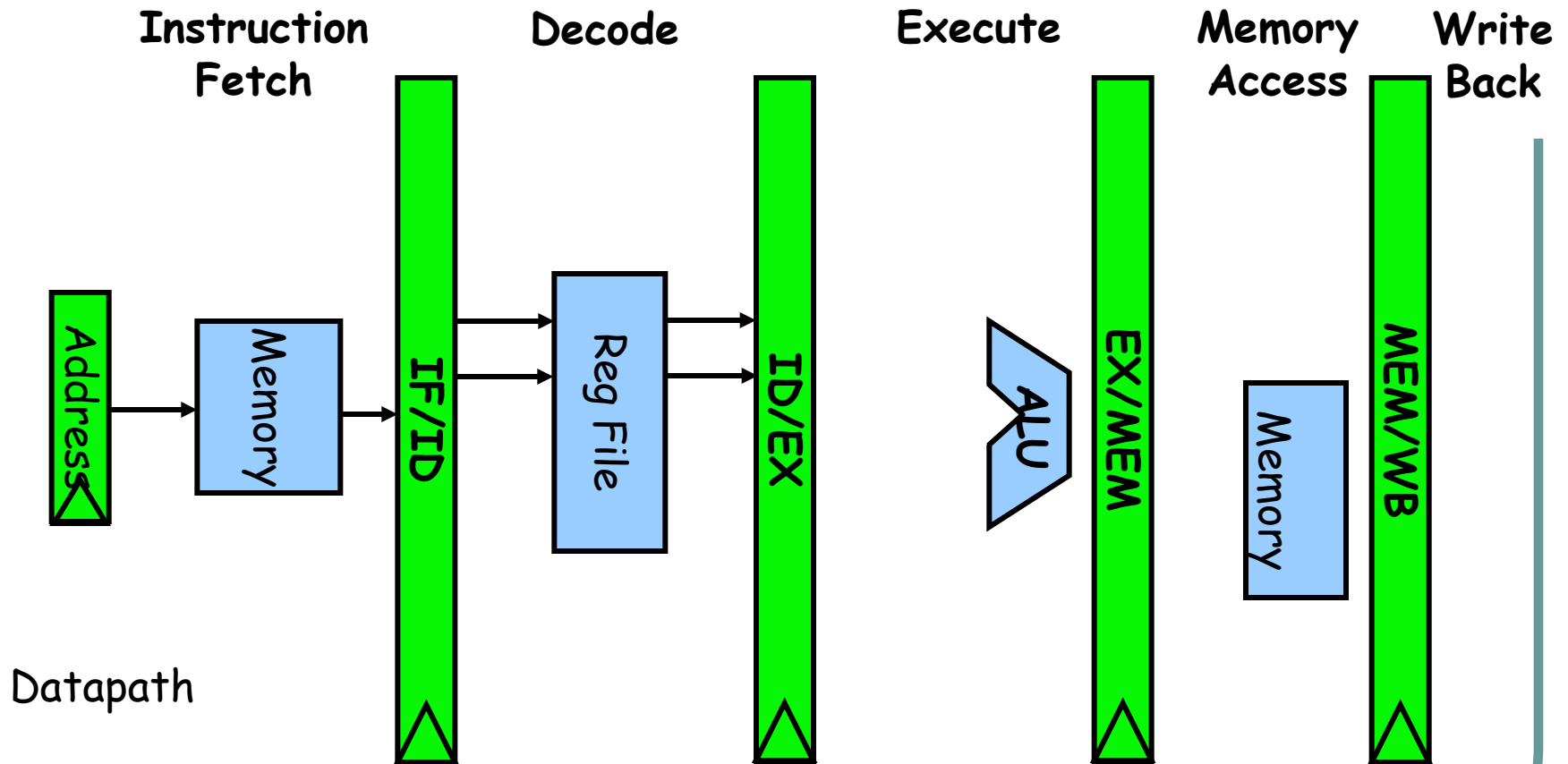


Execution Stage

 


ADD

 


Memory Access

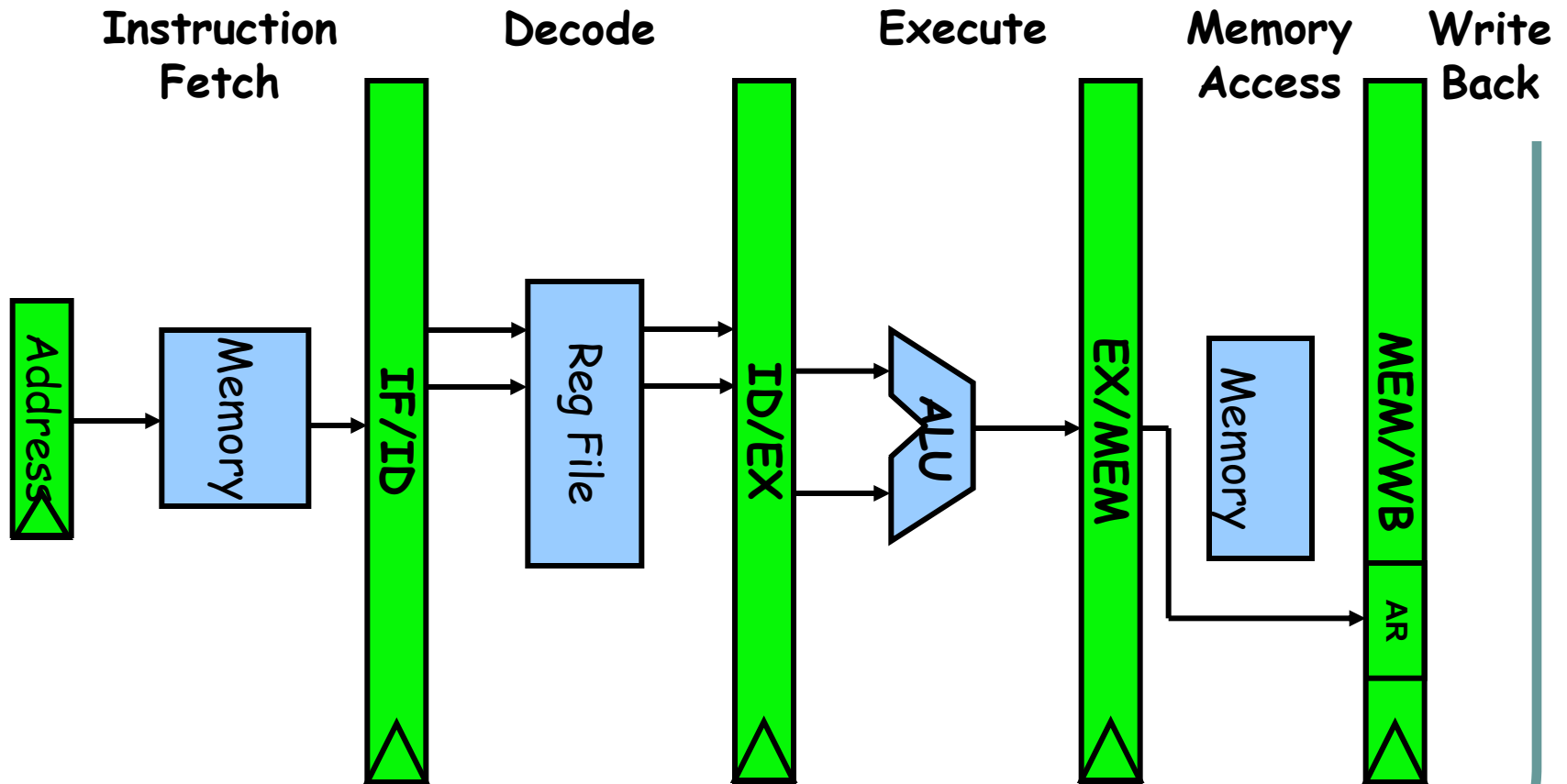

Write Back

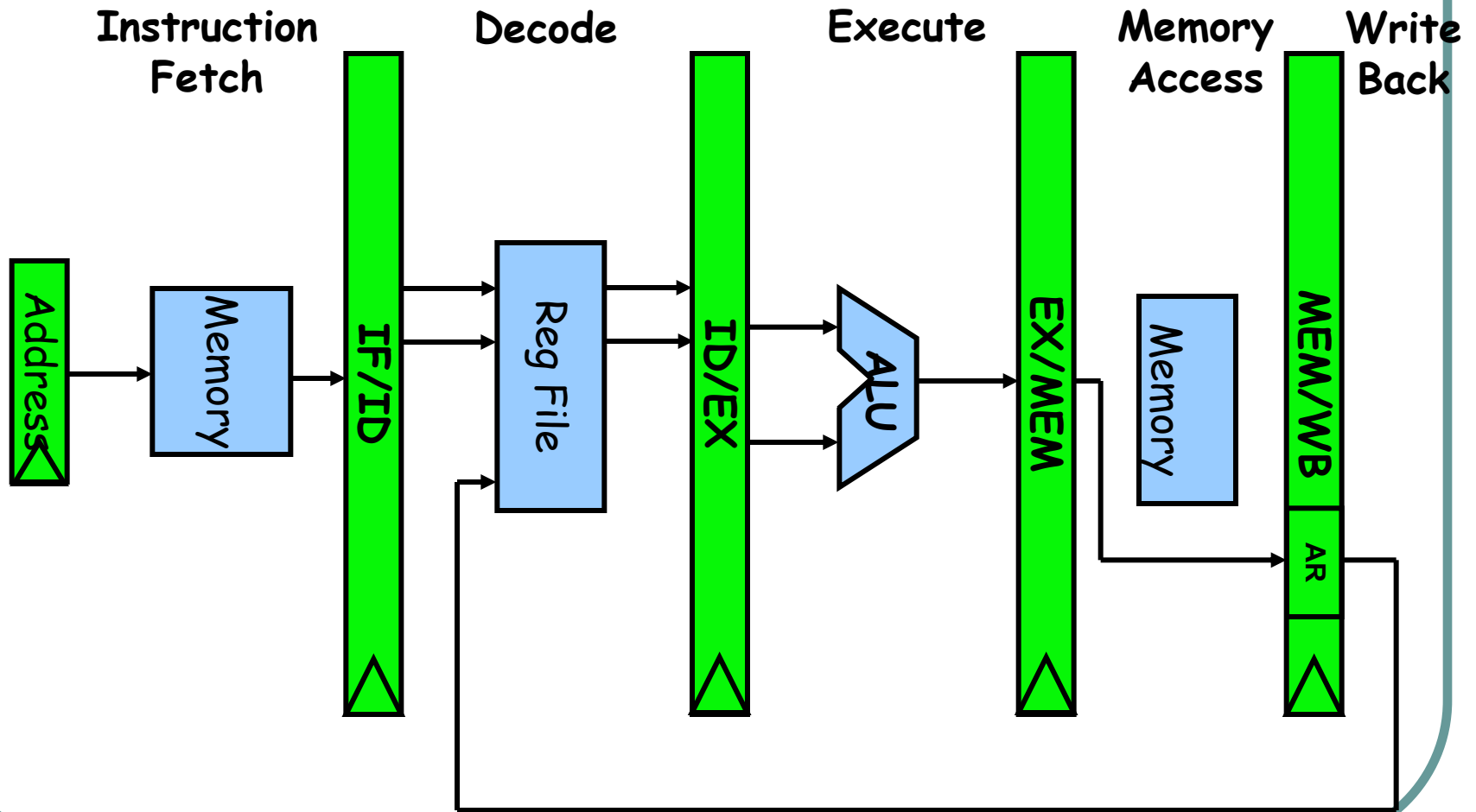


Write Back

 

Write Back


ADD R[2], R[1]

**Write
Back**

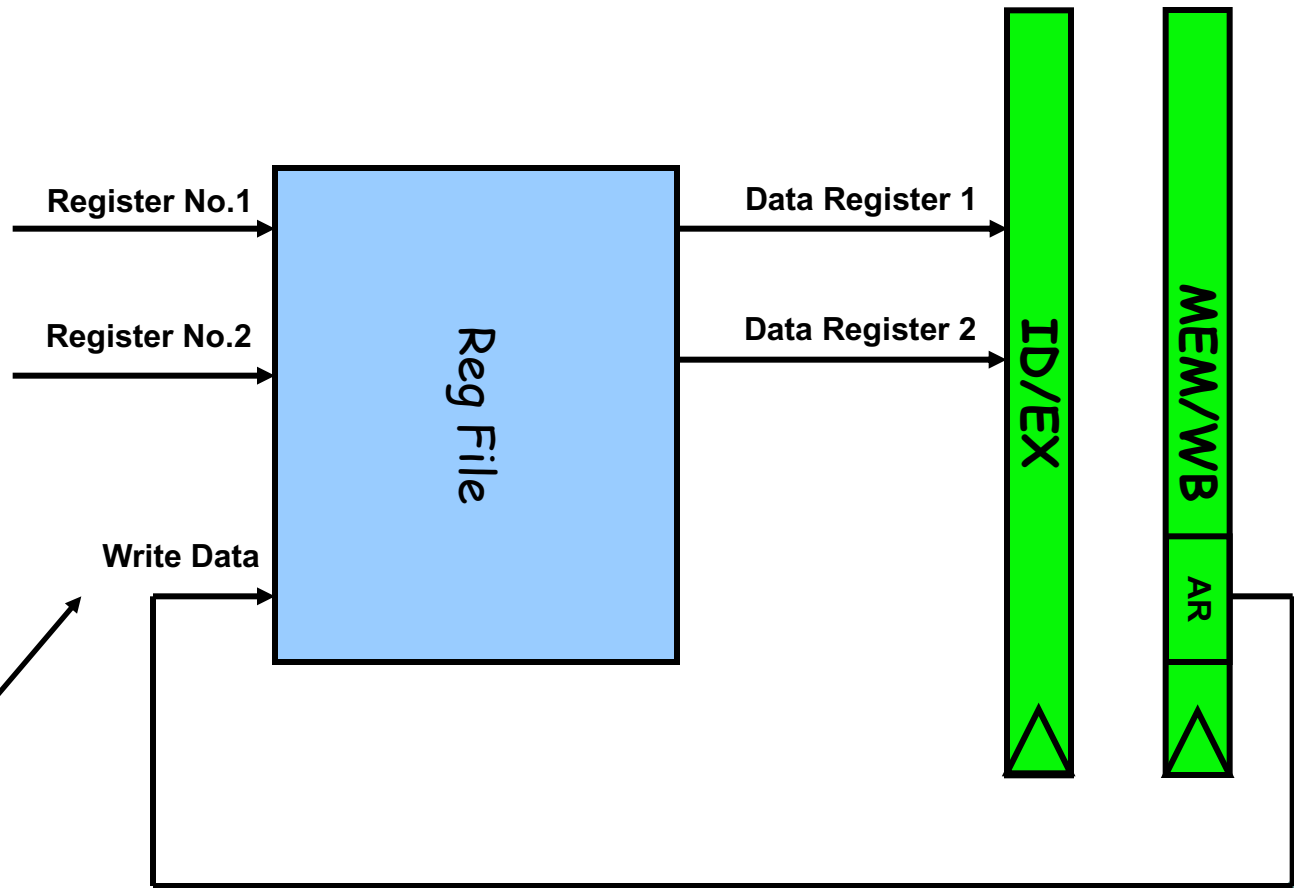


**Which
register**


Revising Our Design

 


Write Back

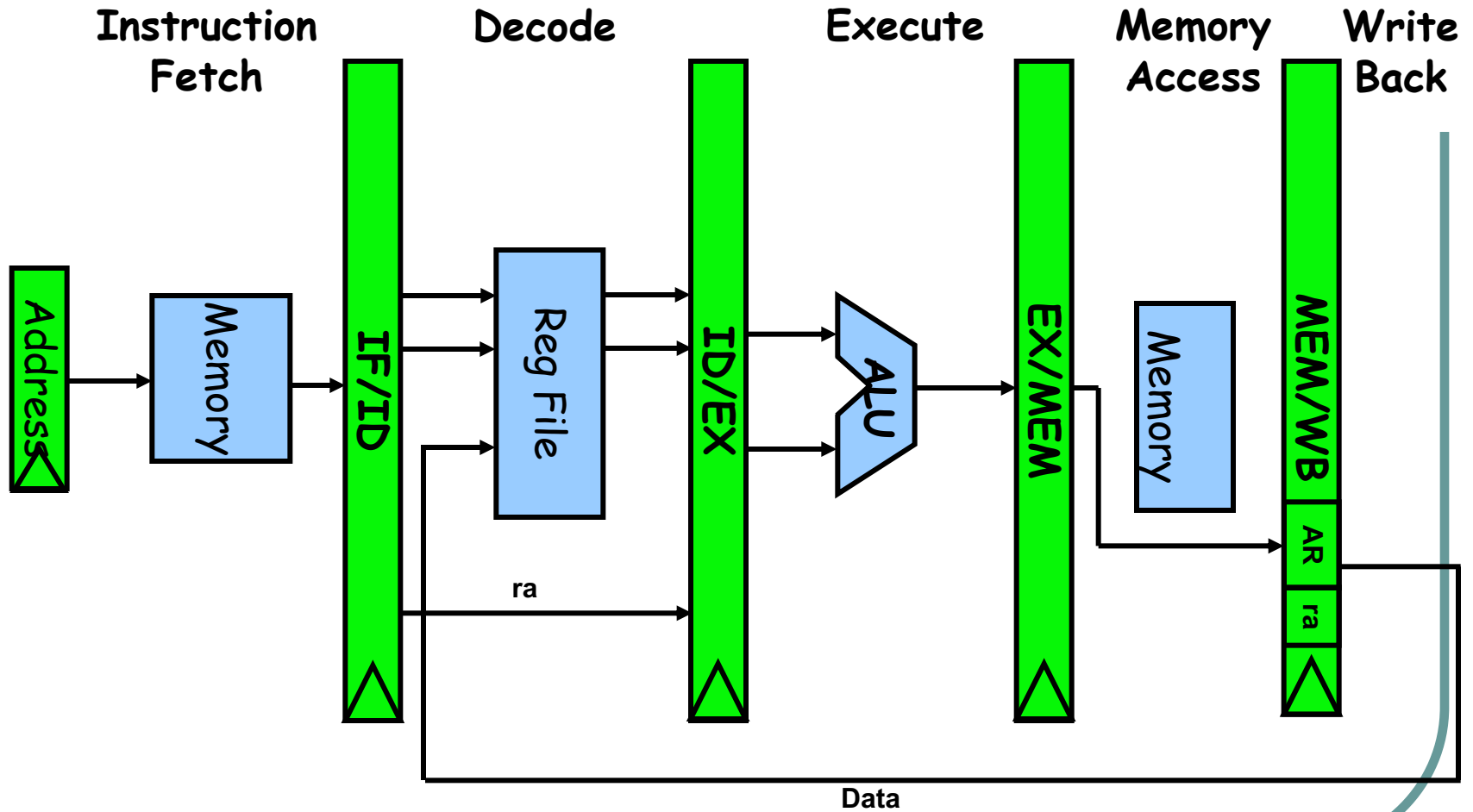


Write Back

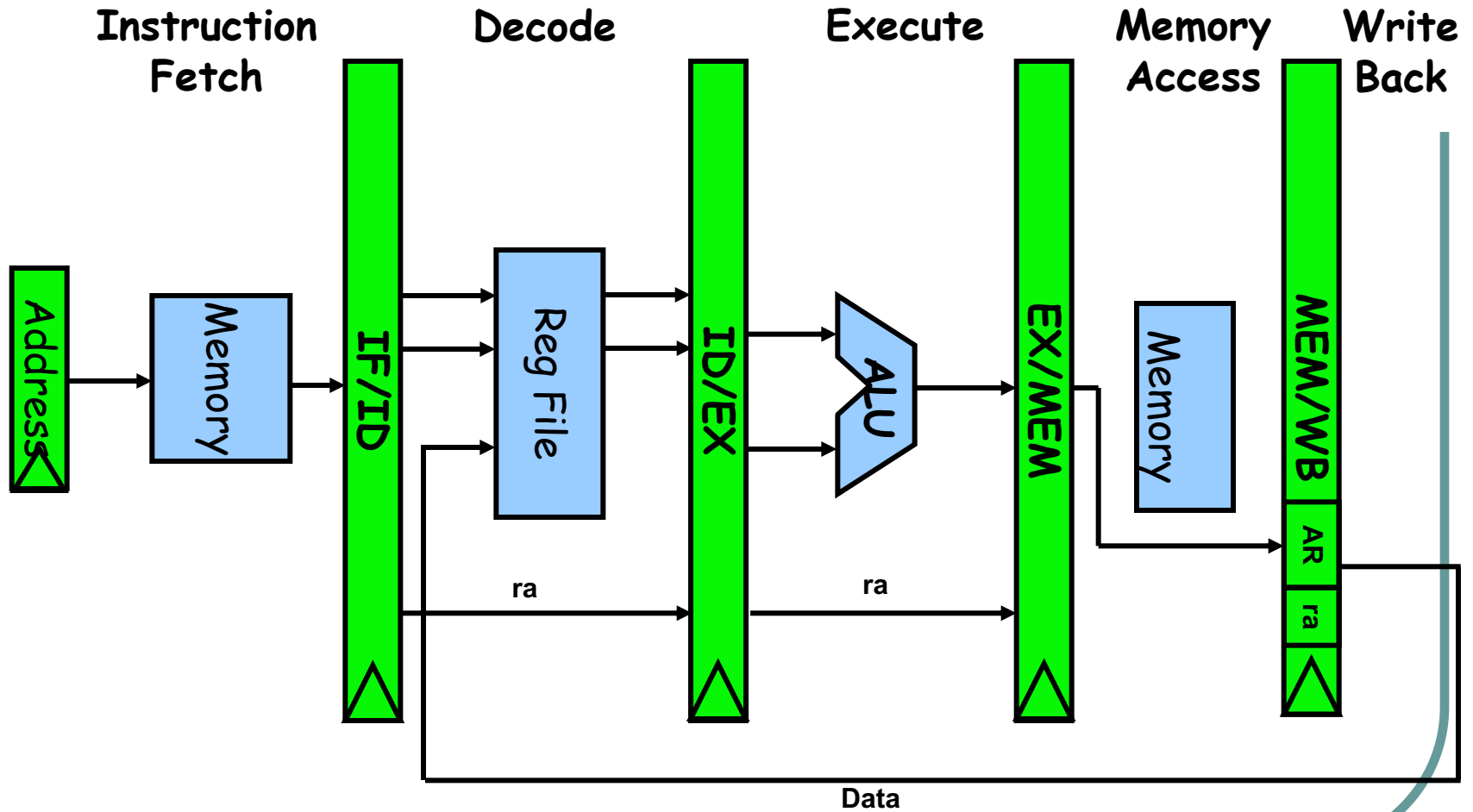

Write Back

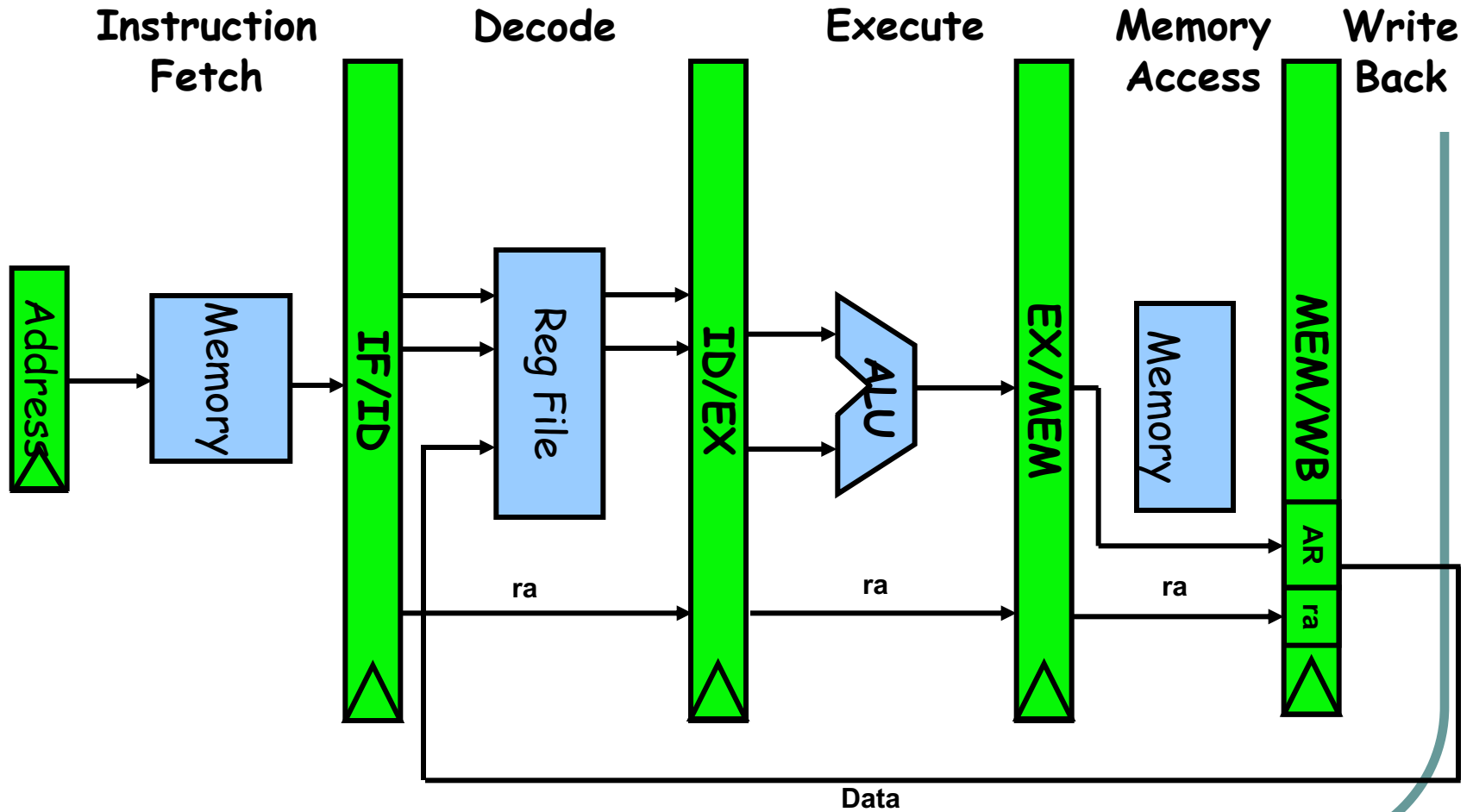


Write Back

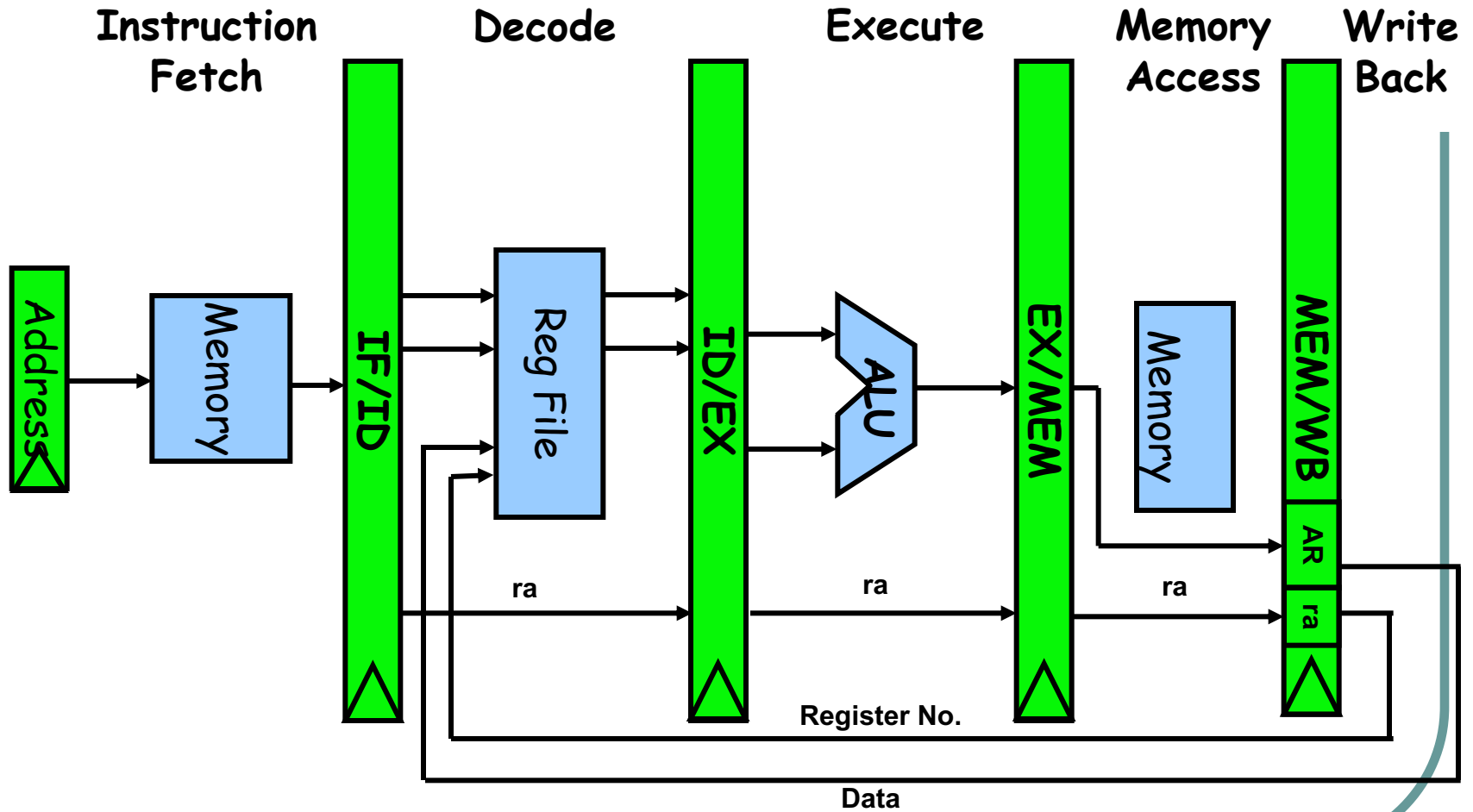

Other Instructions


- We should repeat similar steps for other instructions

Controller

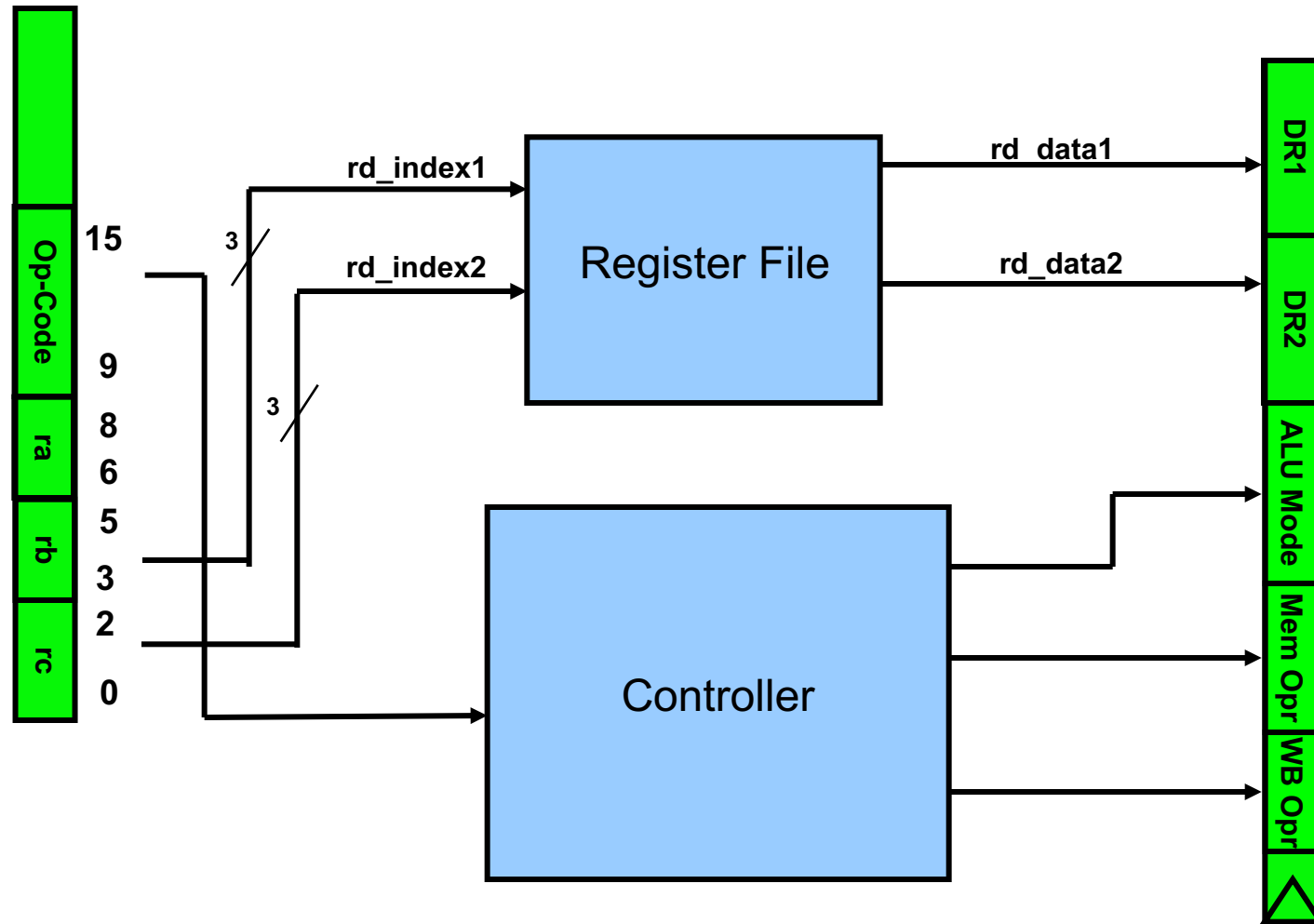


The controller controls all the stages of the pipeline.
It may be distributed, hierarchical or centralized


Execute

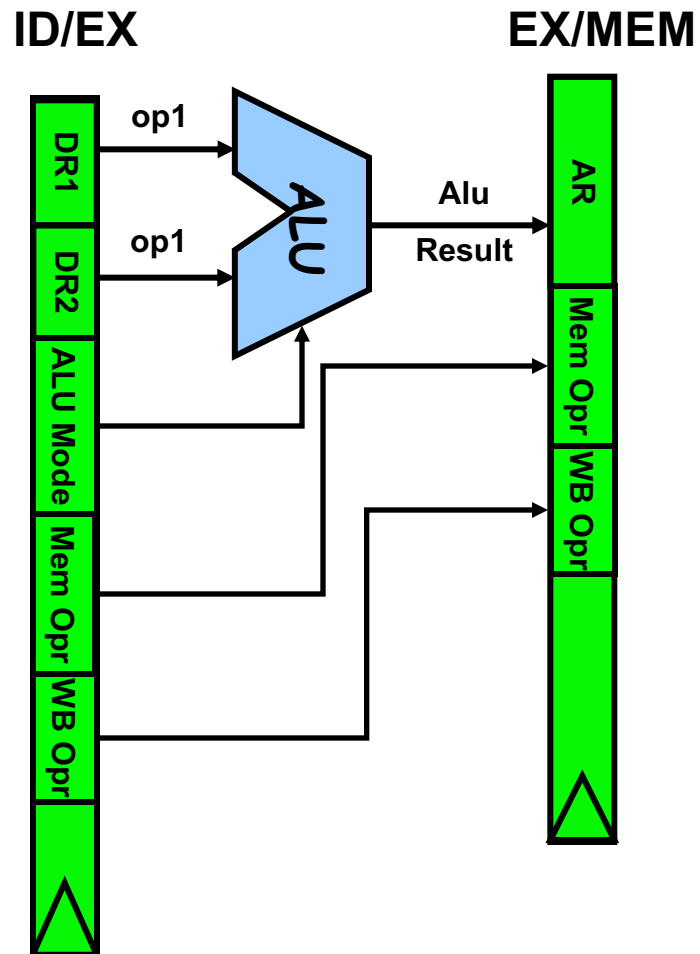

Memory Access

 


Write Back

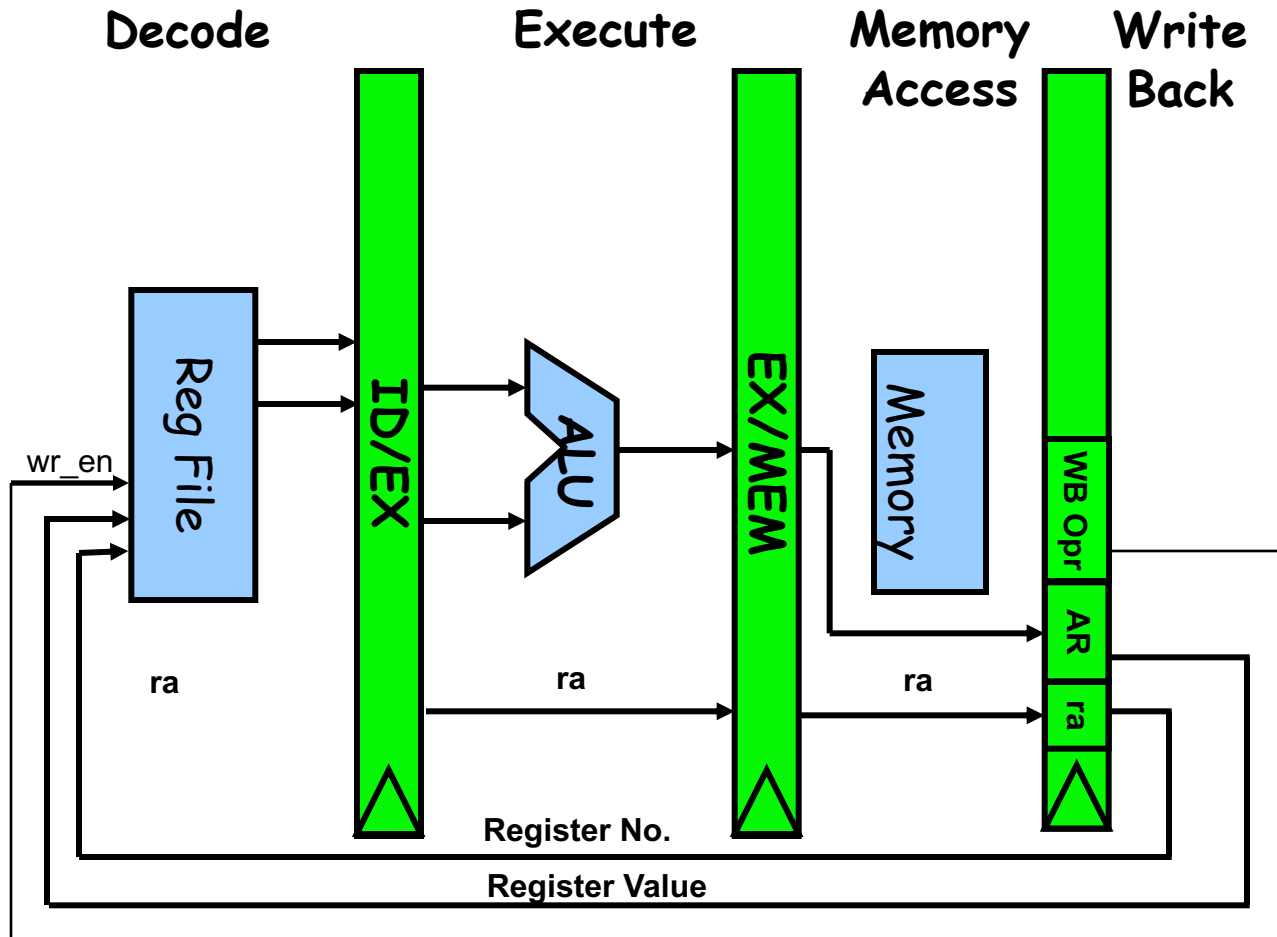


Controller

 Design Controller Base on Control Signals in Data-Path




State Machine

 

State Machine Implementation

```
parameter [3:0]
    RESET=0,DECODE=1;

always @(negedge clk)
    if(rst)
        begin
            state = RESET;
            //deactivate all control signals
        end
    else
        begin
            case(state)
                RESET:  begin
                            state=DECODE;
                        end
                DECODE: begin
                            if(opcode=ADD)
                                ...
                        end
                default:
                    state=RESET;
            endcase
        end
    end
```

 

The reset state needs to be modified to account for the two different resets as per slides 2 & 3

Implementation Strategy


- First Design Datapath
- Design Controller base on Data-Path
- Connect Controller and Data-Path

Designing Datapath

- Necessary Components
 - Program Counter
 - Instruction/Data Memory
 - ALU
 - Register File
 -


Datapath Hierarchy

Start your design from Bottom Modules

 


Simulate each Component

- Post-Route Simulation

 

Wiring CPU (Top Module)

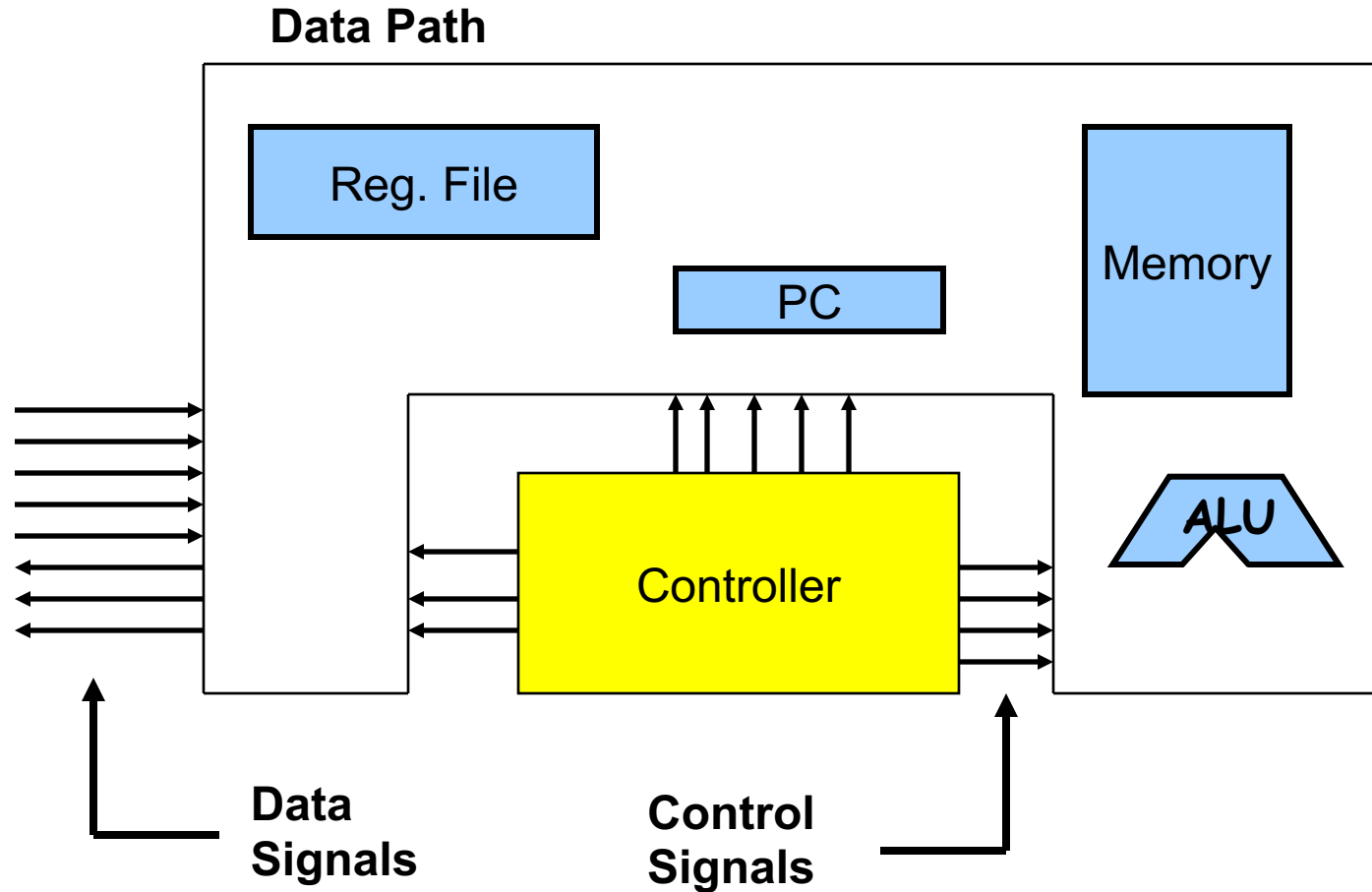

Designing for Hazards

- Hazards Because of Pipeline
 - Data Hazard
 - Control Hazard

Simulate and Implement

- Simulating Complete CPU
- Implementation (Pin Assignment)